Reese Ford Lab 2 – 01/29/2024

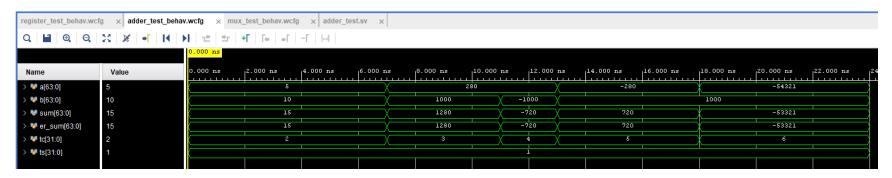


Figure 1: adder_test Waveform

Adder_Test Results ******* BEGIN TEST RESULTS *******

Test Case 1

Inputs: a = 5 | b = 10

+++ Step 1: Pass: |sum| time = 7 ns | er = 15 | ar = 15 | er_bits = 64 | ar_bits = 64 +++

Test Case 2

Inputs: a = 280 | b = 1000

```
+++ Step 1: Pass: |sum| time = 11 ns | er = 1280 | ar = 1280 | er_bits = 64 | ar_bits = 64 +++
Test Case 3
Inputs: a = 280 | b = -1000
+++ Step 1: Pass: |sum| time = 13 ns | er = -720 | ar = -720 | er_bits = 64 | ar_bits = 64 +++
Test Case 4
Inputs: a = -280 | b = 1000
+++ Step 1: Pass: |sum| time = 18 ns | er = 720 | ar = 720 | er_bits = 64 | ar_bits = 64 +++
Test Case 5
Inputs: a = -54321 | b = 1000
+++ Step 1: Pass: |sum| time = 24 ns | er = -53321 | ar = -53321 | er_bits = 64 | ar_bits = 64 +++
Pass Count = 5
Fail Count = 0
***** END TEST RESULTS ******
```

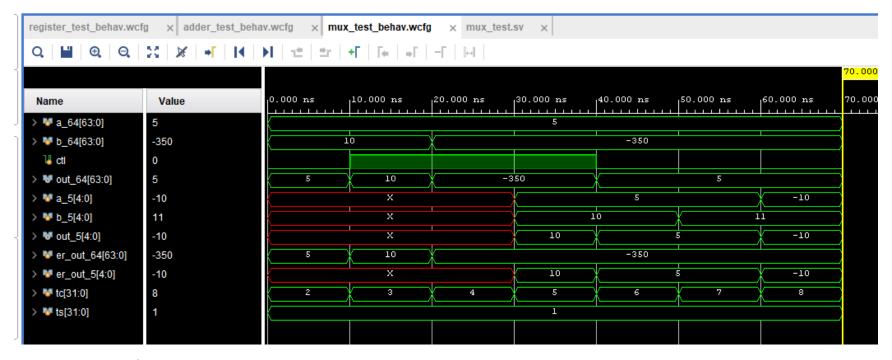


Figure 2: mux_test Waveform

Mux Test Results

****** BEGIN TEST RESULTS ******

Test Case 1

Inputs: a_64 = 5 | b_64 = 10 | ctl = 0

+++ Step 1: Pass: |out_64| time = 1 ns | er = 5 | ar = 5 | er_bits = 64 | ar_bits = 64 +++

```
Test Case 2
```

Test Case 3

Test Case 4

Test Case 5

Test Case 6

```
Test Case 7
```

Inputs: a_5 = 22 | b_5 = 11 | ctl = 0

+++ Step 1: Pass: |out_5| time = 61 ns | er = 22 | ar = 22 | er_bits = 5 | ar_bits = 5 +++

Pass Count = 7

Fail Count = 0

****** END TEST RESULTS ******